

1007ICT / 1807ICT / 7611ICT

Computer Systems & Networks

Assignment Project Exam Help

<https://eduassistpro.github.io/>

3B. Digital Logic and Circuits

Add WeChat edu_assist_pro

Dr. Sven Venema

Dr. Vallipuram Muthukkumarasamy

Last Lecture:

Topics Covered:

- Digital logic, Basic logic gates, Boolean algebra
 - Combinational logic
- <https://eduassistpro.github.io/>
Add WeChat edu_assist_pro

Lecture Content

- Learning objectives
- Logic unit, Selection logic, Decoder logic
- Multiplexing and demultiplexing
- Half and

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro

Learning Objectives

At the end of this lecture you will have gained an understanding of:

- Selection
- Decoder <https://eduassistpro.github.io/>
- Multiplexors Add WeChat edu_assist_pro
- Demultiplexors
- Half and Full adders


Logic Unit

- Lets try to create a “programmable” logic unit that permits us to apply a predefined logic function to a given set of inputs.

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro

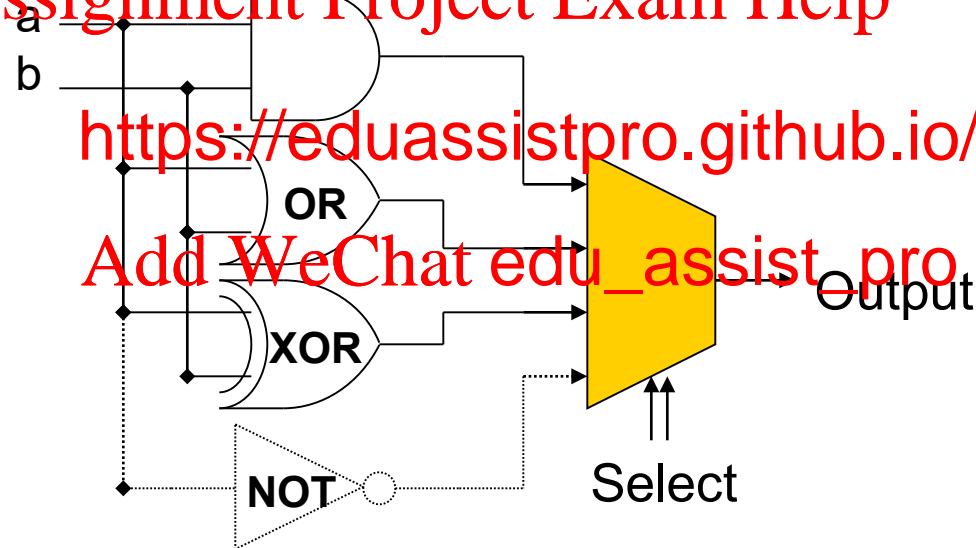


- We need a function that lets us select what operation to perform

Selection Logic

- Say we have a number of inputs 'A,B,C,D' and we want to select one of them to use in a logic function.
- We need a special function to switch the selected input into the output 'X' based on the selection.
- We can select between A-D

<https://eduassistpro.github.io/>

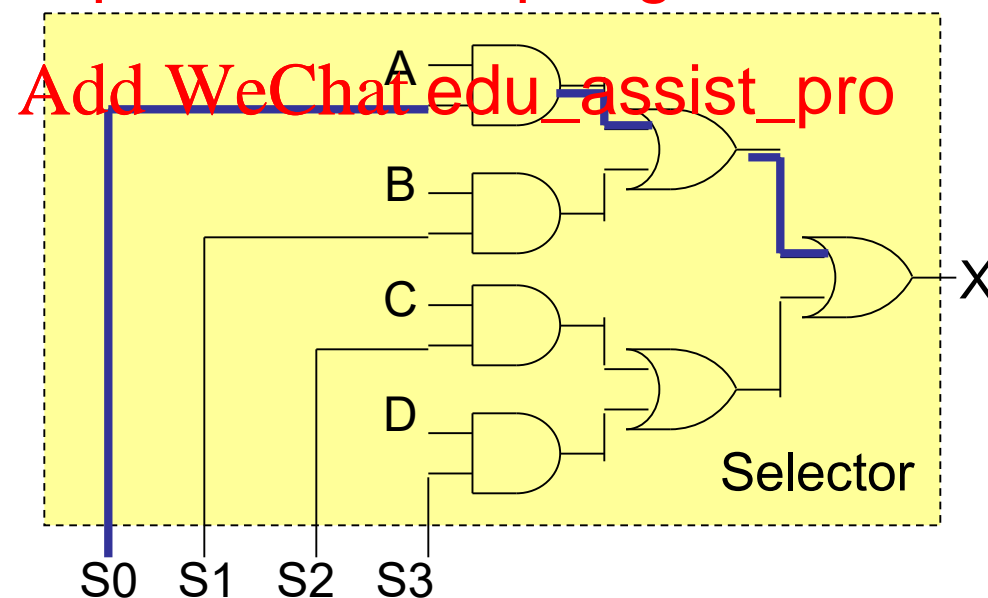

Decoder Logic

- Just say we want to select between one of 100's of possible inputs – we need 100's of selection inputs as well which gets too complicated.
- Decoders with N inputs allow us to enable any one of 2^N possible selection lines.
- Basic and enable inputs for a decoder are used to select any coded number representing the number

Inputs		Outputs			
s1	s2	x0	x1	x2	x3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


2 to 4 Dec

$$x0 = \overline{s1} \text{ AND } \overline{s2}$$

$$x1 = \overline{s1} \text{ AND } s2$$

$$x2 = s1 \text{ AND } \overline{s2}$$

$$x3 = s1 \text{ AND } s2$$

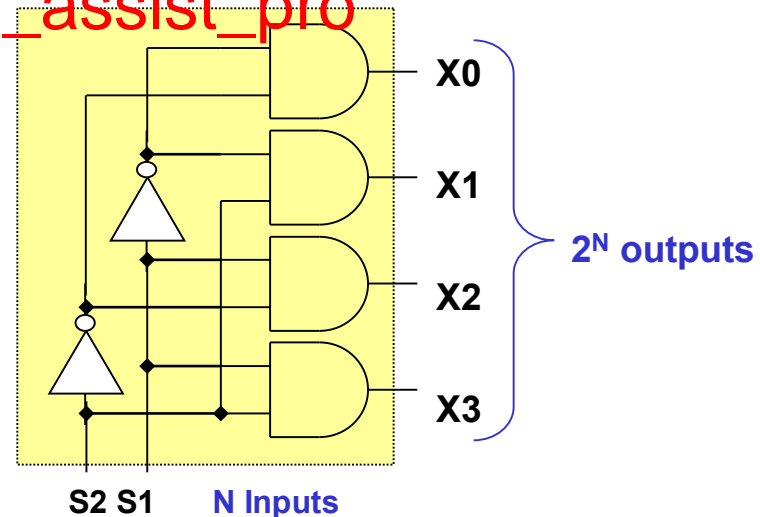

Multiplexing


- Combining the selector and decoder we can create what is called a **Multiplexor**
- In general if we have N inputs we want to switch between we need to have $\log_2(N)$ selection lines.

Assignment Project Exam Help

<https://eduassistpro.github.io/>


Add WeChat edu_assist_pro

s0	s1	X
0	0	A
0	1	B
1	0	C
1	1	D

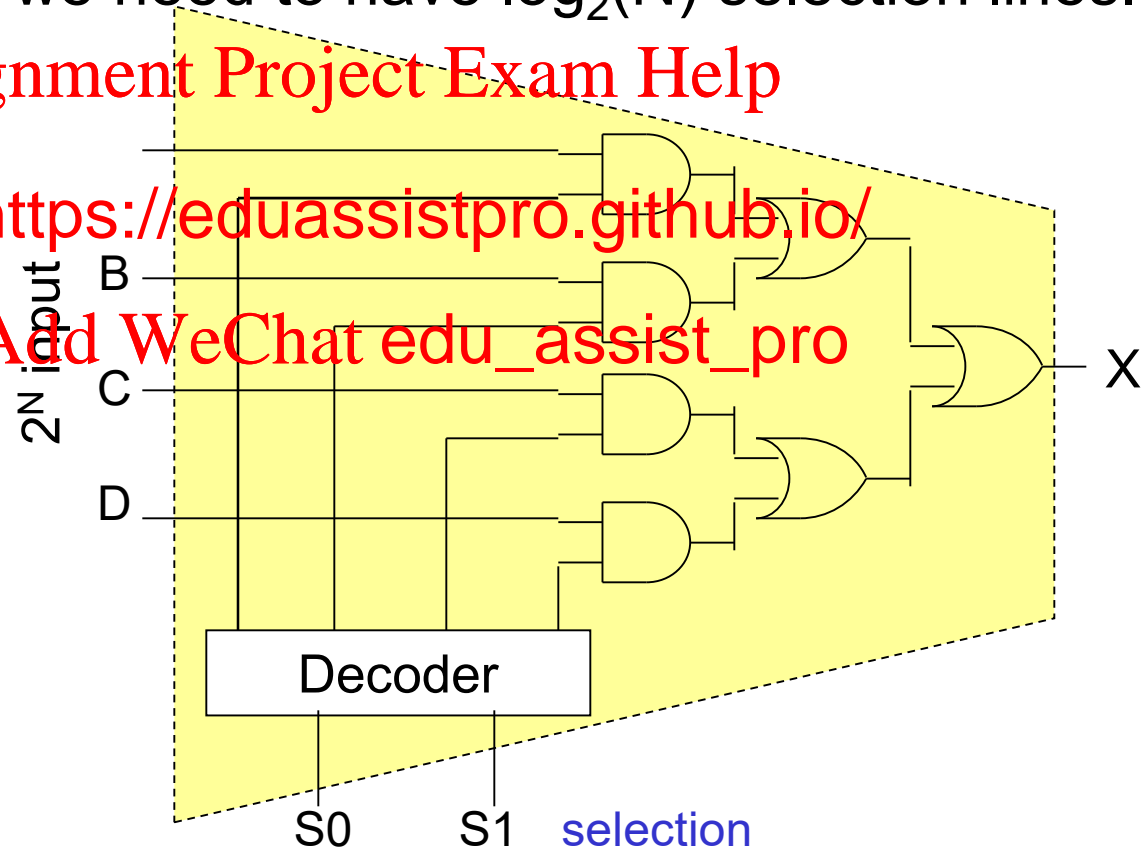

Demultiplexing

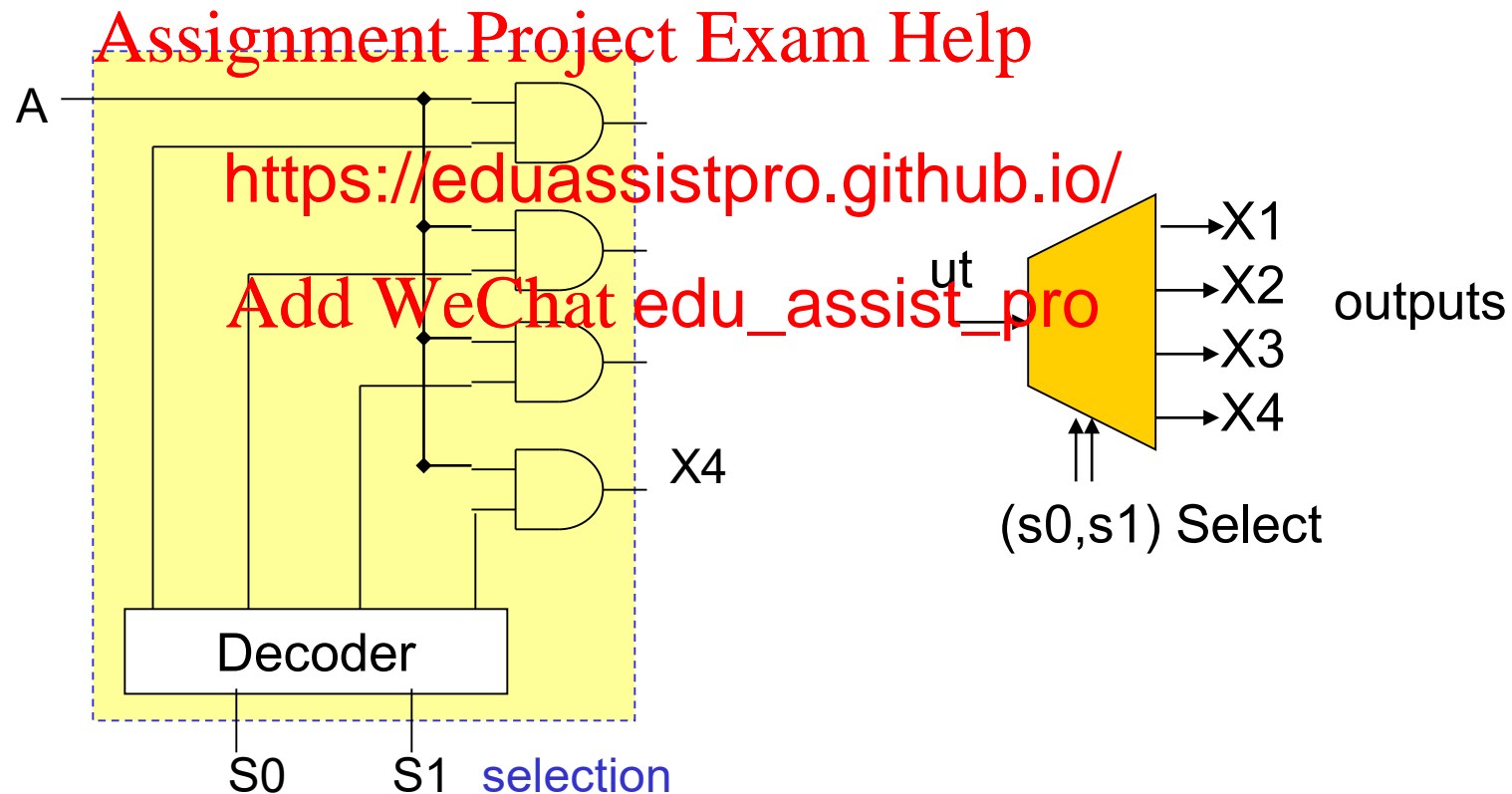
- We can also switch in the opposite direction to send one input 'A' into one of many different outputs (eg X1..Xn)



Half-Adders

- In addition to logic functions we can also create maths functions.
- The simplest math function is the half-adder which can add 2 digits (bits) to give a sum and a

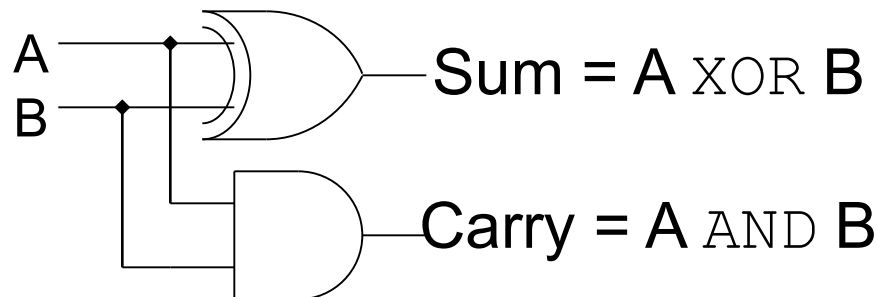
$$\begin{array}{r}
 0 \quad 0 \quad 1 \quad 1 \quad A \\
 0 \quad 1 \quad 0 \quad 1 \quad B \\
 \hline
 0 \quad 1 \quad 1 \quad 10
 \end{array}$$



A	B	Sum	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full-Adders

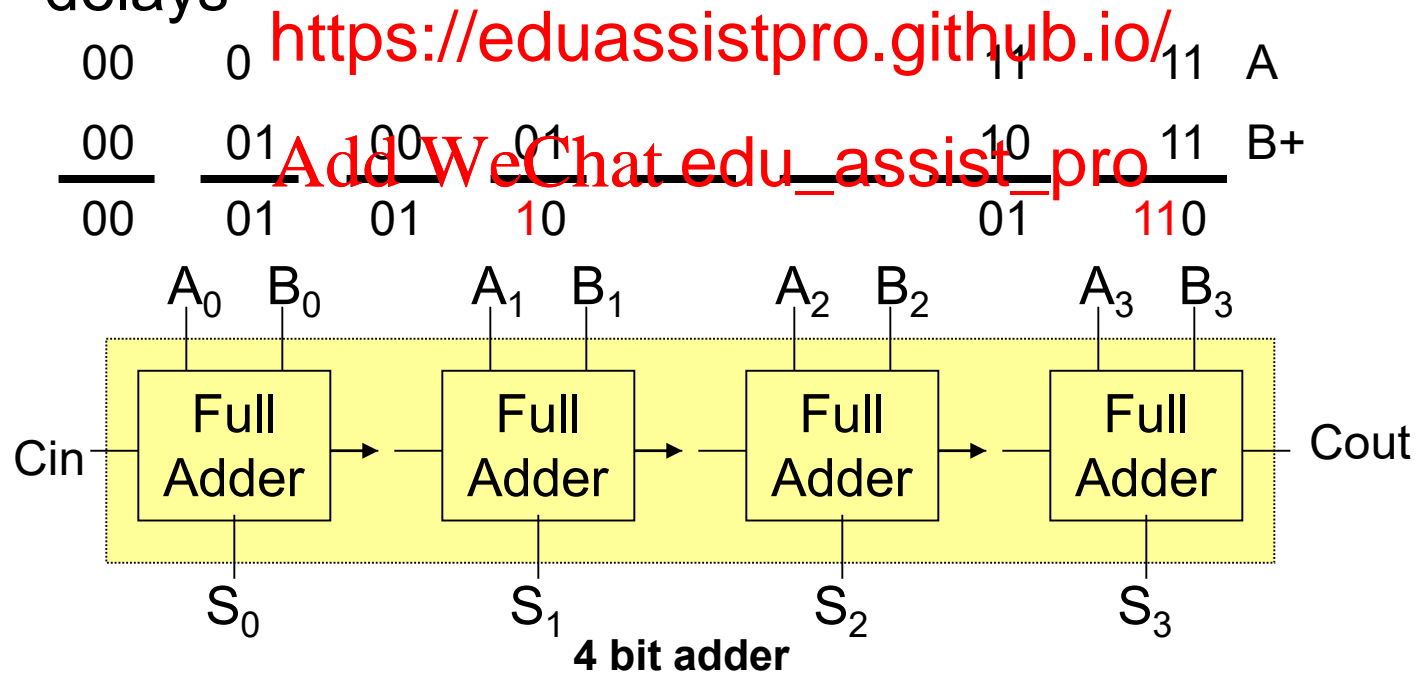- If we want to add more than 1 bit values together we need to deal with the carry.
- Full-adders accept the two inputs to be added plus the carry from a previous stage.
- The circuit must be able to deal with propagation delays



Full-Adders


- The logic to perform add with carry combines two half adders together.

Assignment Project Exam Help

Cin	A	B	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


<https://eduassistpro.github.io/>

Add WeChat: edu_assist_pro

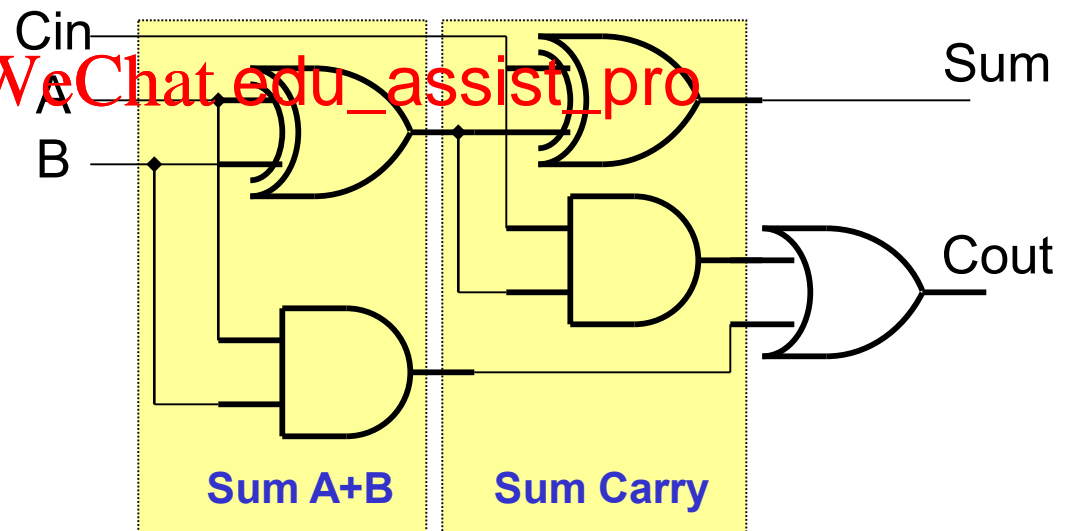

Subtraction

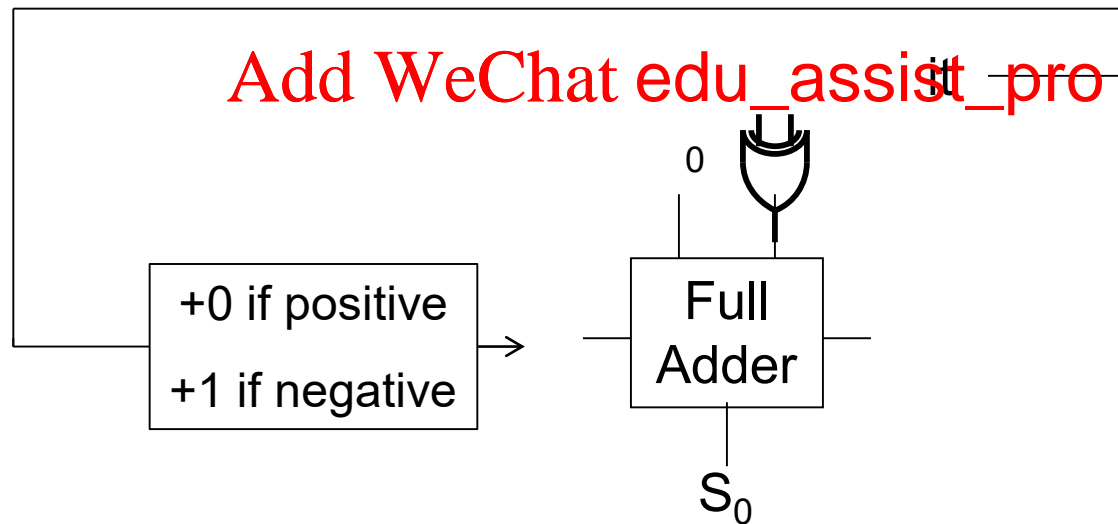- $A - B$ is the same as $A + (-B)$
- If we convert B to the negative equivalent of its value, we can **use the basic adder as it is**. We can use an **XOR** gate to do this.
- However, c two's complement $\text{https://eduassistpro.github.io/}$



Summary

Have considered:

- Selection logic
- Decoder logic
- Multiplex
- Demultip
- Half and Full adders

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro

Next....

- Arithmetic logic unit
- Binary multiplication and division
- Shifting
- **Sequenti**
- Data latches, S-R L
- Clocks and synchronisation
- Registers, Buses, Computer memory
- Processors and Memory Organisation

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro