

1007ICT / 1807ICT / 7611ICT

Computer Systems & Networks

Assignment Project Exam Help

<https://eduassistpro.github.io/>

3C. Digital Logic and Circuits

Add WeChat edu_assist_pro

Dr. Sven Venema

Dr. Vallipuram Muthukkumarasamy

Last Lecture:

Topics Covered:

- Logic un
 - Multiplex
 - Half and Full adders
- Assignment Project Exam Help
coder logic
<https://eduassistpro.github.io/>
ing
Add WeChat edu_assist_pro

Lecture Content

- Learning objectives
- Arithmetic logic unit
- Binary multiplication and division
- Shifting
- Sequential
- Data latch
- Clocks and synchronisation
- Registers, Buses, Comput

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro


Learning Objectives

At the end of this lecture you will have gained an understanding of:

- Arithmetic logic unit
- Binary multiplication
- Shifting
- Sequential Logic
- Data latches, S-R Latch
- Clocks and synchronisation
- Registers, Buses, Computer memory


ALU – Arithmetic Logic Unit (Section 7.2)

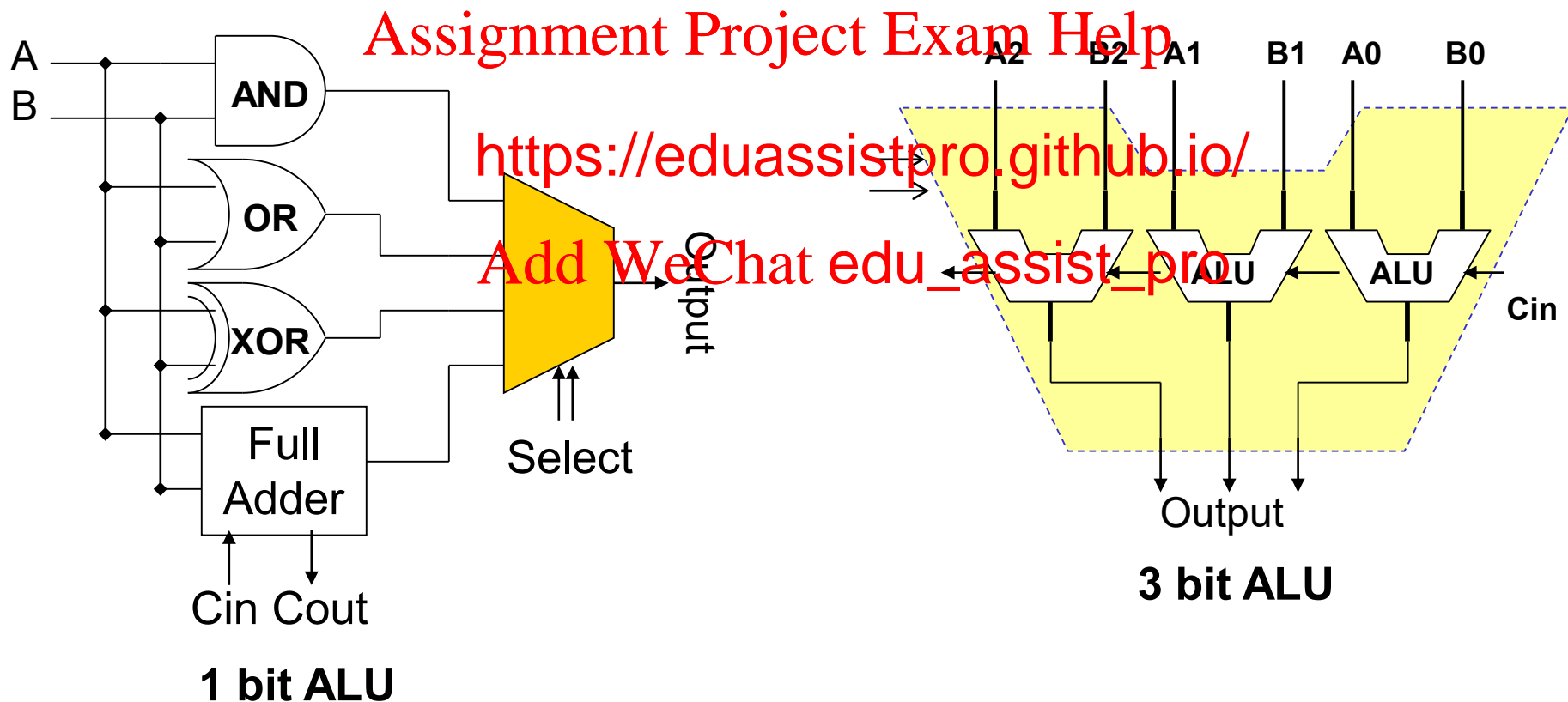- The ALU is a general processing element
- It puts everything we have learnt together
- ALUs are combined in parallel for multi-bit versions



Multiplication and Division By 2

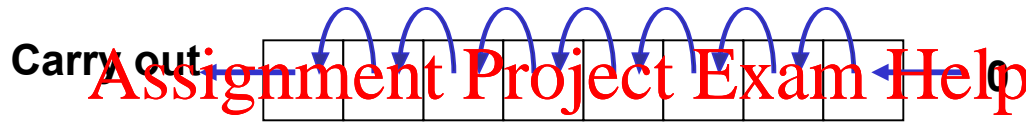
- To multiply by 2 in binary, shift bits left and insert a zero at the right hand side.



$$\begin{aligned} 0001_2 &= 1_{10} \\ 0010_2 &= 2_{10} \\ 0100_2 &= 4_{10} \end{aligned}$$

<https://eduassistpro.github.io/>

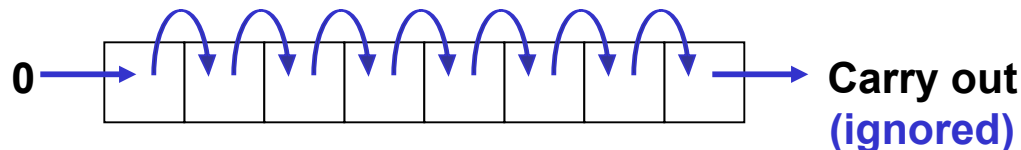- To divide by 2 in binary, shift bits right and insert a zero at the left hand side.





$$\begin{aligned} 0111_2 &= 7_{10} \\ 0011_2 &= 3_{10} \\ 0001_2 &= 1_{10} \end{aligned}$$

Shifters

- We can use multiplexors to shift bits left and right.
- We need to select each output bit to be the input bit on its left or right side


Assignment Project Exam Help

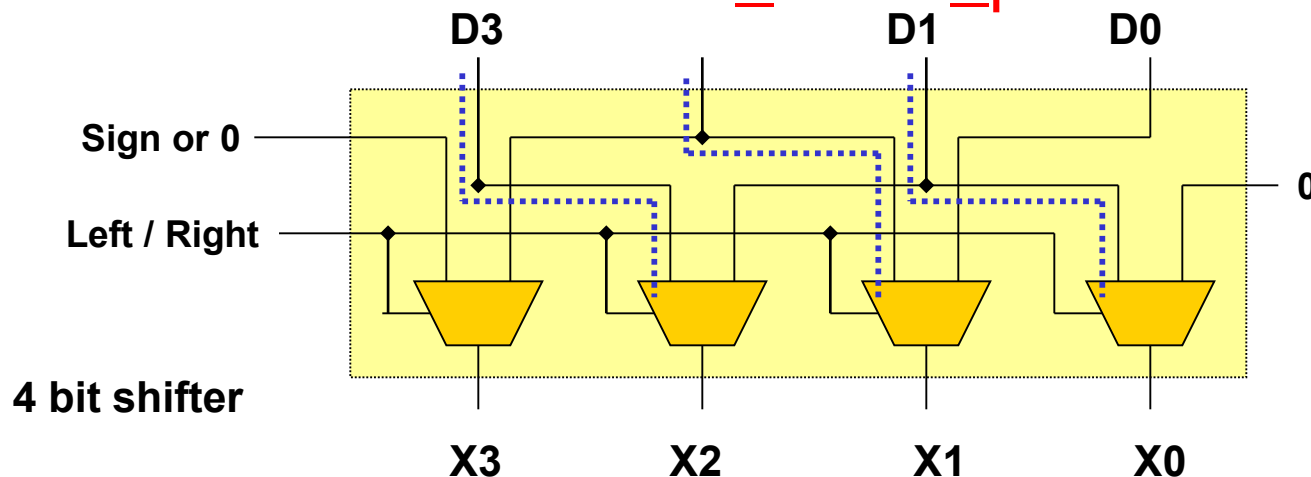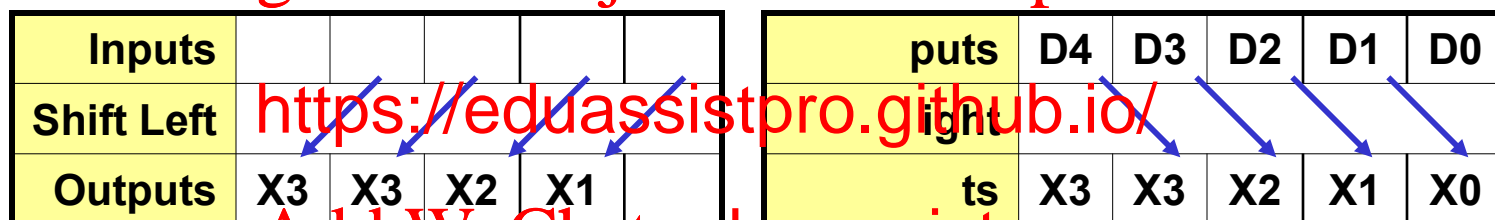

Shifters

- What if we also want the shifter to not shift or to set the output to zero? Use a 4-input multiplexor

SEL	Out
00	Zero
01	Right
10	Left
11	Thru

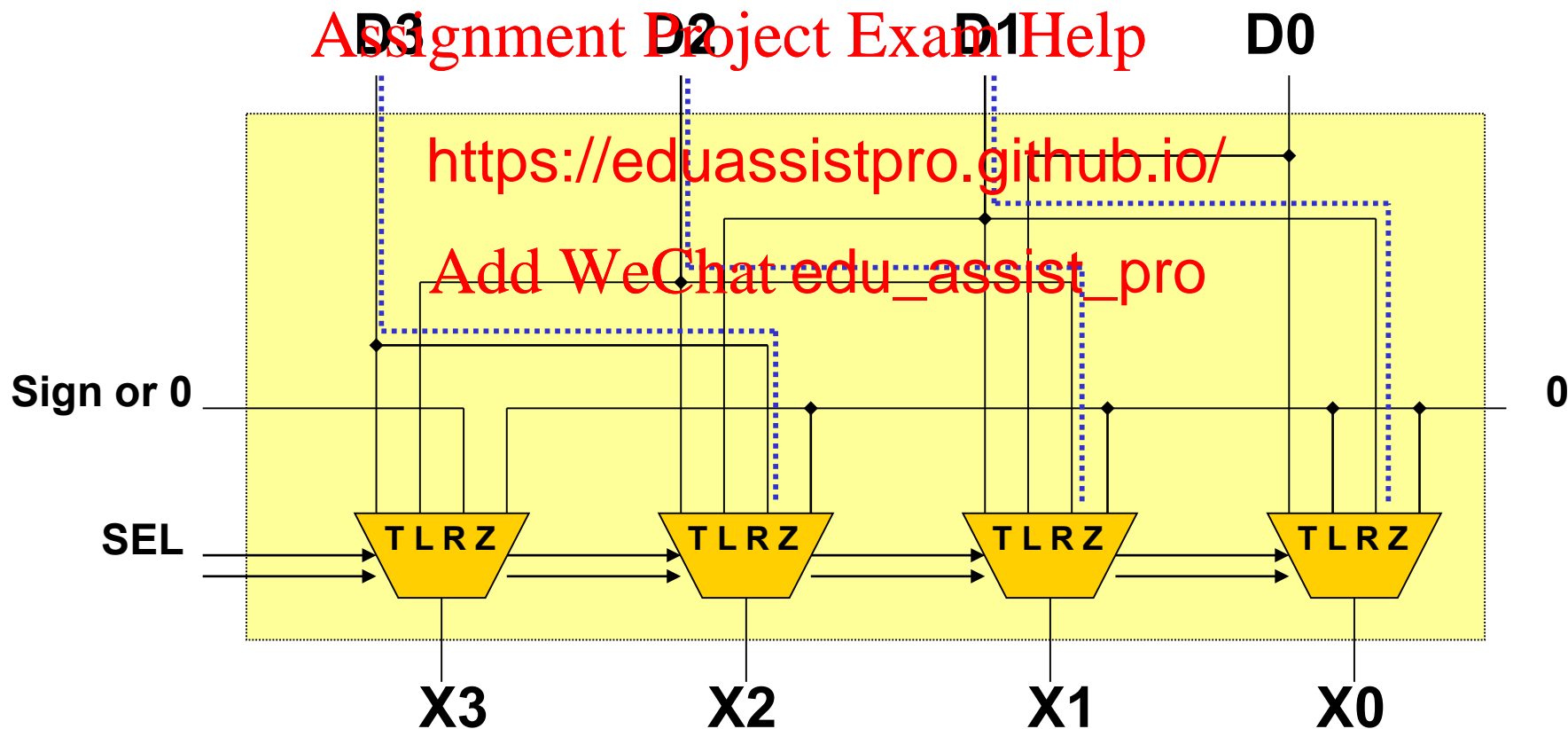

Arbitrary Multiplication

- To multiply by other numbers say $A * B$ – we could add A to itself B times, but it's faster to use shifts and adds like this...
- The powers of 2 you need to add to get the multiplicand determines the number combination of shifts and addition we need to perform on the multiplier (ie the 1s in its binary value)

Assignment Project Exam Help

- Let \ll denote the binary left shift operator.

- $10 \times 5 = ($

$$\begin{aligned} 5 &= 101_2 \\ &= 100_2 + 1_2 \\ &= 4 + 1 \end{aligned}$$

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro

	fts	Binary	Hex
	$\ll 2$	101000	28
10×1	$1010 \ll 0$	001010	0A

- $10 \times 7 = (10 \times 4) + (10 \times 2) + (10 \times 1) = 1000110_2$

$$\begin{aligned} 7 &= 111_2 \\ &= 100_2 + 10_2 + 1_2 \\ &= 4 + 2 + 1 \end{aligned}$$

Mult.	Shifts	Binary	Hex
10×4	$1010 \ll 2$	101000	28
10×2	$1010 \ll 1$	010100	14
10×1	$1010 \ll 0$	001010	0A

Multiplication Example

Multiply $\text{Sum} \leftarrow A \times B$

- Check every bit position of B so that if:
 - bit position 0 of B is 1, add A to the sum.
 - bit position 1 of B is 1, add $A \ll 1$ to the sum.
 - bit position 2 of B is 1, add $A \ll 2$ to the sum.
 - bit position 3 of B is 1, add $A \ll 3$ to the sum.
 - etc..

$$10 \times 13 = 130$$

$$1010_2 \times 1101_2$$

<https://eduassistpro.github.io/> *is not added as*

bit p *01₂ is 0.*
Add WeChat edu_assist_pro

$$\begin{array}{rclcl}
 & & \rightarrow & 1010_2 & \ll 0 & \text{-----} & 1010_2 \\
 & & \rightarrow & 1010_2 & \ll 2 & \text{-----} & 101000_2 + \\
 & & \rightarrow & 1010_2 & \ll 3 & \text{-----} & 1010000_2 + \\
 & & & & & & 10000010_2 = 130
 \end{array}$$

Arbitrary Division

- For arbitrary division we can use basic binary long division.

$$\begin{array}{ccccccc}
 & & & 8 & 4 & 2 & 1 & & 2 & 1 \\
 13 & / & 3 & = & 1 & 1 & 0 & 1 & / & 1 & 1 \\
 & & & = & 4 & \text{Remainder } 1
 \end{array}$$

Assignment Project Exam Help

<https://eduassistpro.github.io/>

$$\begin{array}{r}
 11 \overline{) 1101} \\
 \underline{- 11} \\
 001 \rightarrow \text{Remainder: } 1
 \end{array}$$


Add WeChat edu_assist_pro

Sequential Logic (Section 2.5)

- Previously we looked at **combinatorial** logic which produces an output as some combination of the input values.
- Sequential** logic produces an output that depends on previous outputs but on

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro

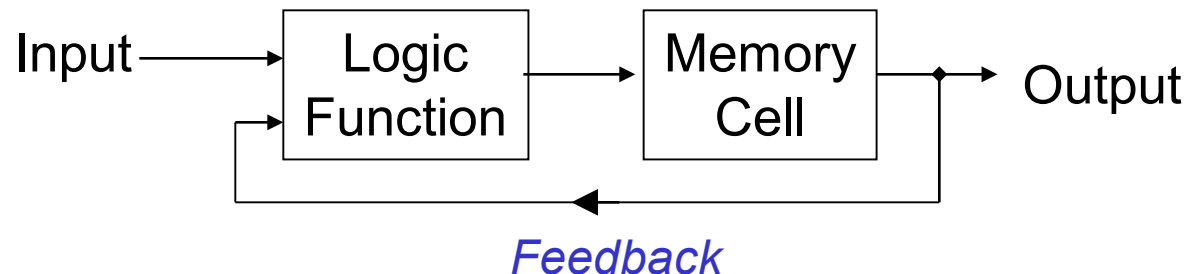


Data Latches

- None of the logic functions we saw before can store any data... bits come in and go straight out again.
- A **Latch** is a logic function that can store bits
- Consider the following logic:




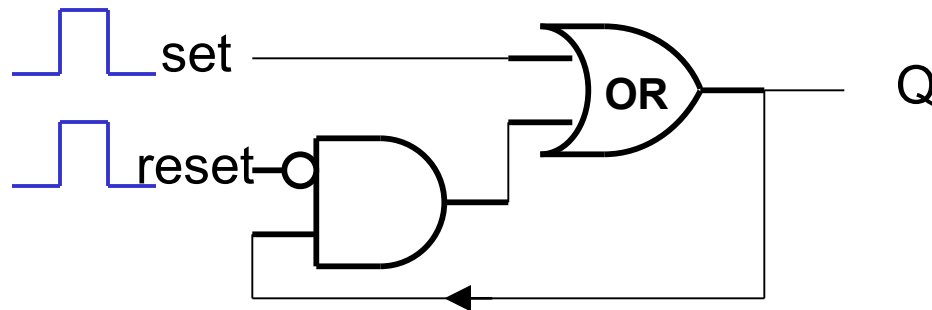- This can store a '1' bit but we need another input to tell it to store a '0' bit, like this.




S-R Latch (RS-Bistable)

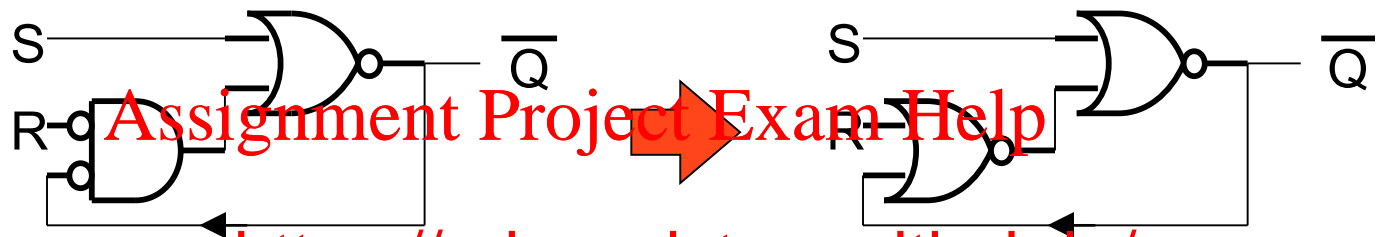- Let's rearrange the logic a bit as follows using the rules of logic (using DeMorgan's Theorem) :




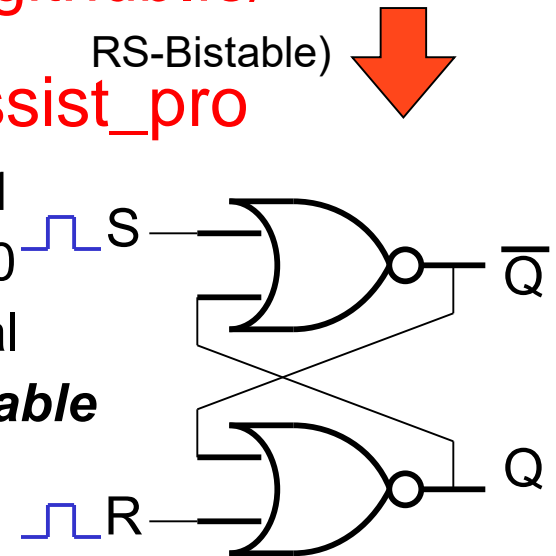- The result is called the RS-Bistable)
 - Both inputs are normally
 - The S input sets the data state to 1
 - The R input sets the data state to 0
 - Having both to ON at once is illegal
 - When both are OFF the latch is **stable**
 - Either $Q = 0$ and $\bar{Q} = 1$
 - Or $Q = 1$ and $\bar{Q} = 0$



Clocks and Synchronisation



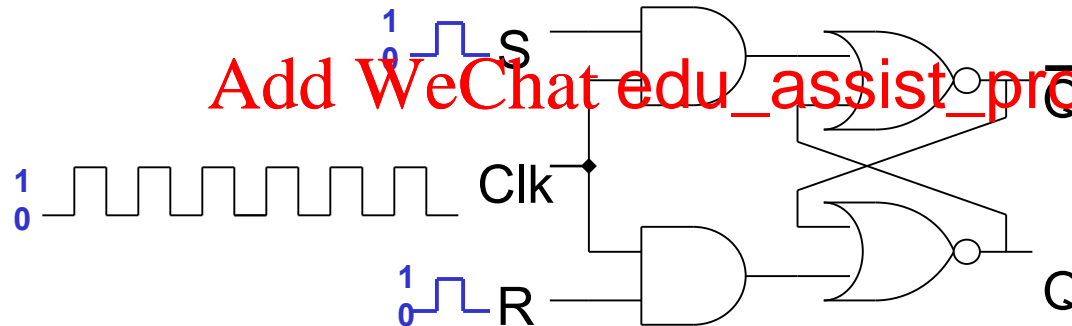
- The main problem with latches is that after the inputs change the output is unstable for a short time.
- If we directly connect the output of a latch to the input of another circuit then the circuit may be unstable
- A clock signal can control when a latch can load its inputs after (when the clock is high)



- Clocked latches are sometimes called **Flip-Flops**;
- The faster the clock – the faster that data can be stored/read into a latch

Data Latch (Level-Triggered D-Type bistable)

- We can use DeMorgan's Theorem again to convert the Latch to use NAND gates that is set using OFF inputs.
 - Both inputs are normally ON
 - Setting S to OFF sets the data state to 1
 - Setting R to OFF sets the data state to 0
 - Having both S and R OFF sets the data state to 0
 - When both S and R are ON, the data state remains unchanged
- A simple modification of the SR Latch version lets us create the useful **D-Latch**

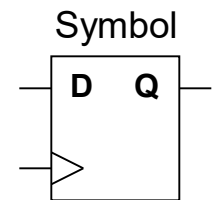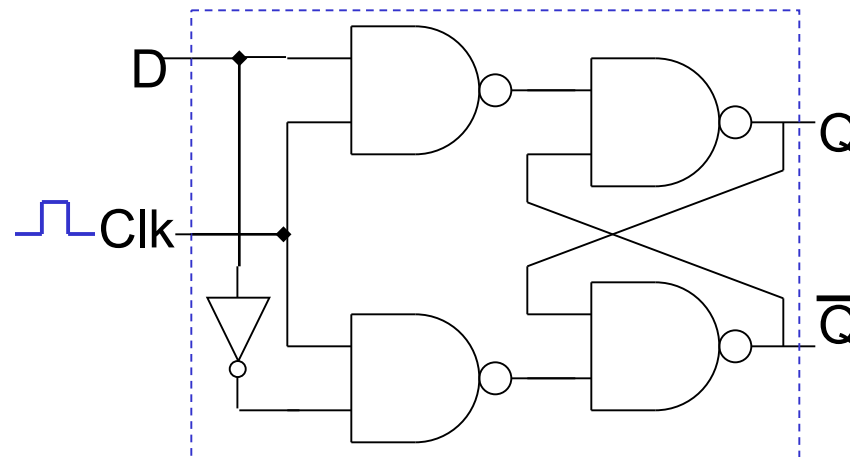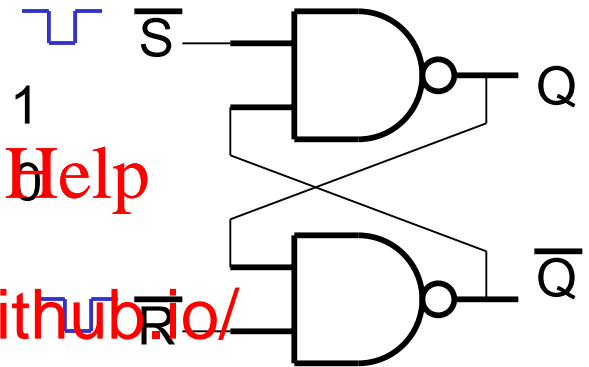

Bits / Bytes / Words

- If computer memory was only addressed one bit at a time, it would take quite a long time to retrieve enough data to any serious processing.
- Most computers do not process individual bits but instead group them together into multiples of 8 eg 8, 16, 32, <https://eduassistpro.github.io/>
- These groups are described as **bytes**, but word length varies depending on the architecture.
- An 8 bit word is called a **Byte**.
- A 4 bit word is called a **Nibble** so 1 byte = 2 nibbles
- There are no special names for other sized words.



Registers

- Data Latches (Level-Triggered D-Type bistables) allow us to store 1 bit of information but we can group them in parallel
- This is called a **register** to store data consisting of multiple bits.
- The **words** bits a register can store

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro

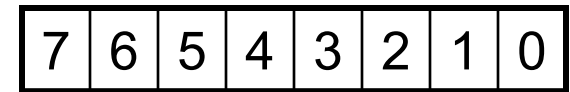
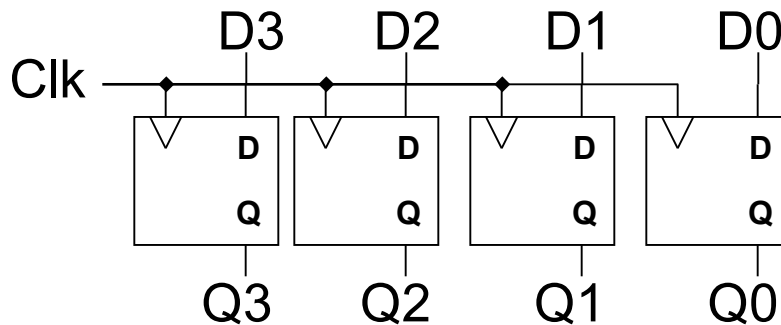


8 bit register

Simple 4 bit register using D-Latches

Buses

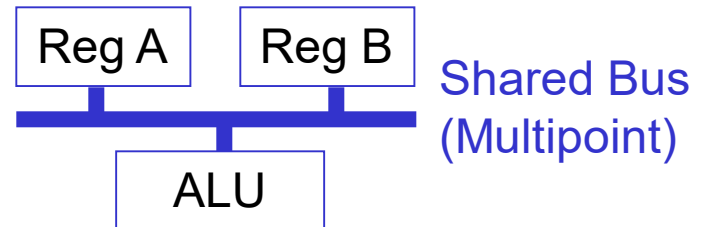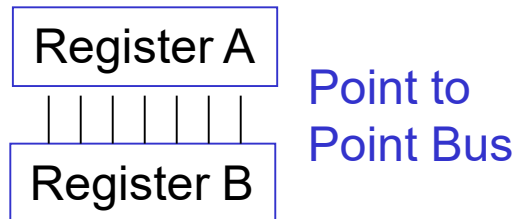- We can connect logic gates together with lines that convey single bits of information between them.
- With registers we have multiple input and output lines to convey N-bits of data to and from the register
- A **bus** is a set of lines that simultaneously conveys a set of bits
- Two types in computer systems: **point-to-point** and **shared bus (multipoint)**.



Multipoint Buses use special gates with “tristate” outputs that can be connected together

Computer Memory (Section 3.3)

- We can use an array of registers in series to create a memory bank.
- Every register location in the memory bank is given a unique address that is used so that we can select it and access the data stored in it.
- An 8 bit memory bank of 8 bit registers and access any at a time.

Add WeChat edu_assist_pro

Fetching word at address 003
would return the value
 $01100100_2 = 64_{16} = 100_{10}$

assist_pro

	Bit							
	6	5	4	3	2	1	0	
005	1	0	0	1	1	0	0	
004	0	0	0	0	1	0	1	
003	0	1	1	0	0	1	0	
002	0	0	0	0	0	0	0	
001	1	1	1	1	1	1	0	
000	0	0	1	1	1	1	1	


Computer Memory

- A memory bank needs some way of selecting memory addresses
- A special register called a memory address register (**MAR**) which is internal to the CPU contains the physical location of the next memory address that will be selected for reading/writing.
- Another internal register called the Memory Buffer Register (**MBR**) [or Memory Data Register (**MDR**)] holds the value that was read /written to the selected memory address.

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro

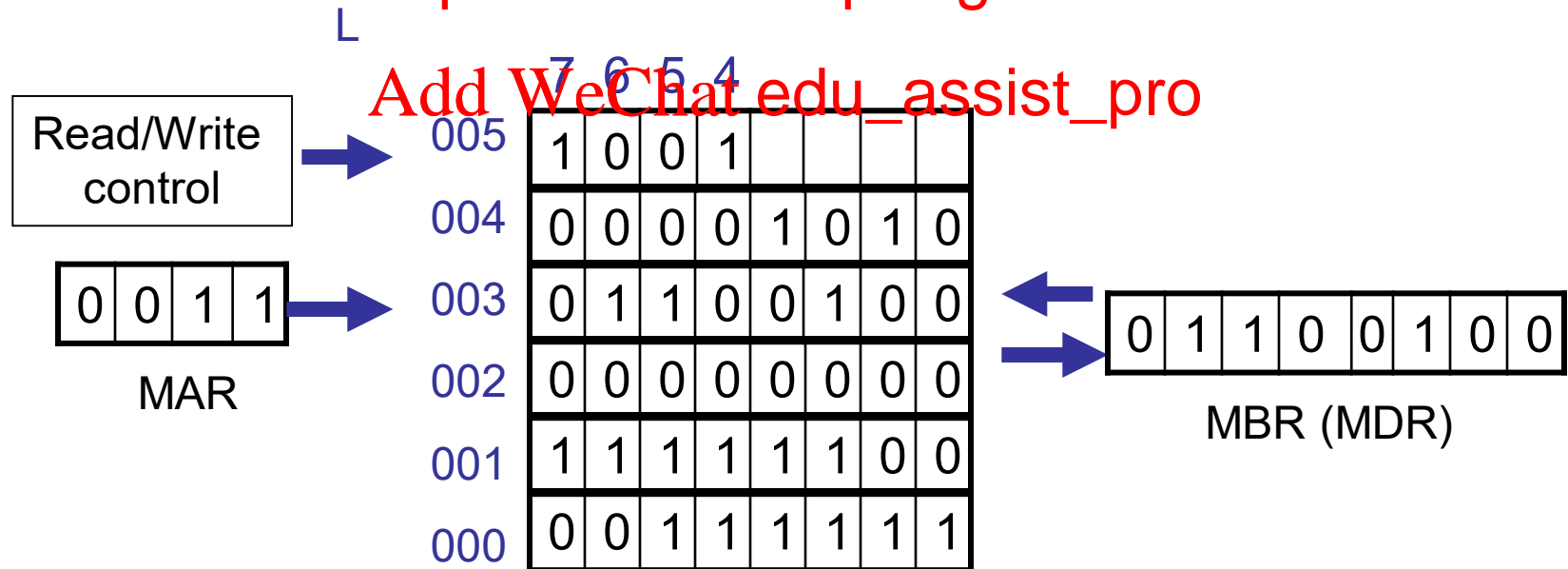

Summary

Have considered:

- Arithmetic logic unit
- Binary multiplication and division
- Shifting
- Sequential
- Data latches, S-R Latch
- Clocks and synchronisation
- Registers, Buses, Computer memory

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat: edu_assist_pro

Next....

- Processors

Assignment Project Exam Help

<https://eduassistpro.github.io/>

Add WeChat edu_assist_pro